
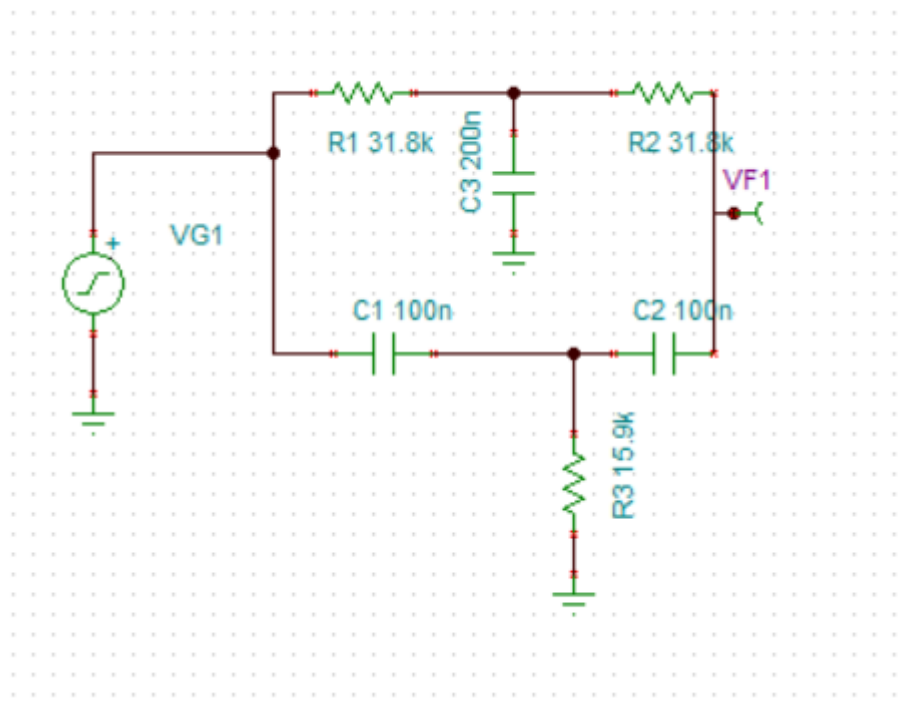


The Twin-T Notch Filter as the name suggests , is composed of two T-type networks, a high-pass part composed of resistors and capacitors, and a low-pass part composed of capacitors and resistors, formed in parallel.

The primary function is to generate a deep notch at a specific frequency, effectively eliminating interference signals of targeted frequencies, such as 50Hz power line interference.

Simulation from TINA

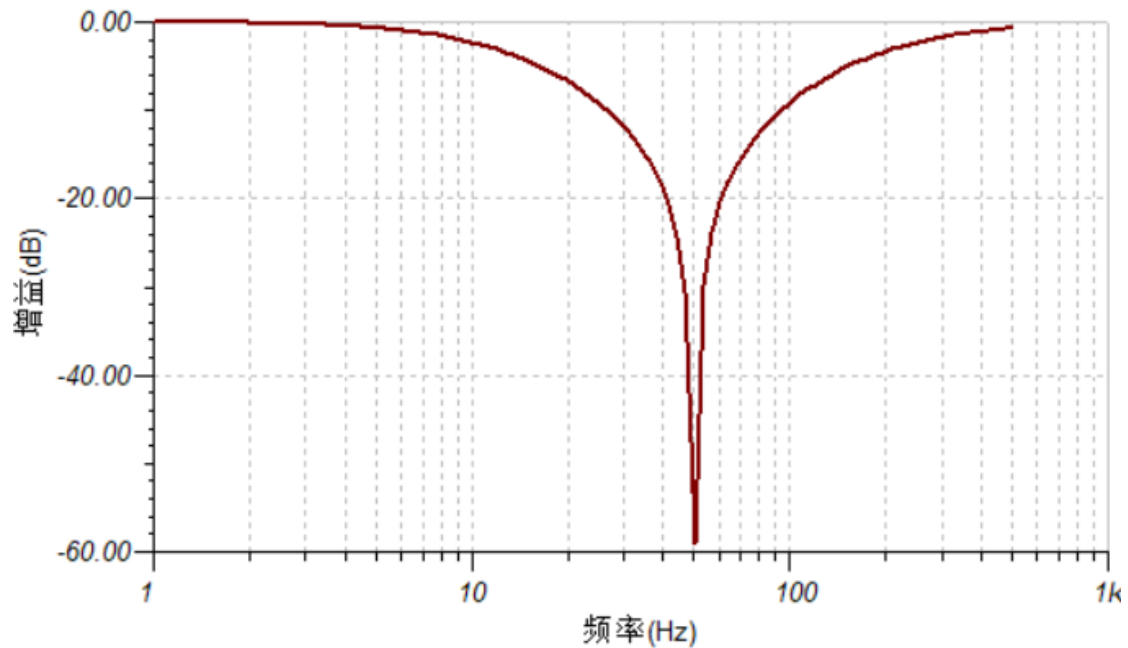



The resistor and capacitor for The Twin-T Notch Filter should follow these steps:

- 1) **Determine the frequency f_0**

$$f_0 = 1/(2\pi R C)$$

*In this document, the target frequency is **50Hz**.*

- 2) **Select standard capacitor values**

Prioritize commonly available capacitor values for practicality.

Example: If $C=100$ nF, substituting into the formula yields

$R \approx 31.8$ k Ω .

- 3) **Match component ratios**

The standard Twin-T structure requires the following ratios:

- a) Upper T-network: 2 resistors R and 1 capacitor $2C$

(E.G., 31.8k Ω +31.8k Ω +200nF)

b) Lower T-network: 2 capacitors C and 1 resistor R/2

(E.G., 100nF+100nF +15.9kΩ)

Ensure strict adherence to these ratios, as deviations will degrade notch depth and frequency response.

Strictly speaking, **this filter is a passive Twin-T filter**. Its key advantage is simplicity, but it suffers from a low Q factor (limited frequency selectivity)

If you need a high Q factor, consideration should be given to using an **active Twin-T notch filter**, which will be detailed in a separate document.

Additionally, when implementing a passive Twin-T notch filter in practical applications, it is critical to ensure impedance matching between the circuit and adjacent stages. If the load impedance is low (e.g., with ADCs, speaker, etc.), a buffer stage (such as a voltage follower) must be added to prevent loading effects from degrading the notch filter's performance. This buffered configuration essentially constitutes an active Twin-T notch filter.

*The **Q** factor (Quality factor) is defined as the ratio of the notch filter's center frequency f_0 to its stopband bandwidth Δf .*

- a) High Q value: Narrow stopband bandwidth, enabling the notch filter to suppress signals within an extremely narrow frequency range. This achieves precise elimination of single-frequency (e.g., 50Hz power line interference).*
- b) Low Q value: Wide stopband bandwidth, suppressing signals across a broader frequency range but with reduced rejection depth.*